

No. of Printed Pages : 4
Roll No. .

120828

HSBTEonline.com

2nd Sem. / Comp, ECE, I&C, Med. Eltx, Power Eltx.

Subject : Basic of Electrical Engg.

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1
- Unit of Voltage is _____.
 - Instrument used for measuring current is _____.
 - Rate of doing work in electric circuit is _____.
 - When temperature increases resistance of wire _____.
 - If R_1 and R_2 are resistance connected in series then total resistance = _____.
 - According to kirchhoff's current law the algebraic sum of currents meeting at junction is equal to _____.
 - An ideal voltage source has _____ resistance.

(1)

120828

HSBTEonline.com

- In lead Acid battery anode is made of _____.
- Primary cell can be recharged. True/False.
- Define M.M.F.
- Unit of inductance is _____.
- Flux is measured in _____.
- Define frequency.
- Define form factor.
- In pure inductor current lags behind voltage by a phase angle of _____.
- Unit of Impedance is _____.
- Series resonance in R-L-C circuit occur when $X_L =$ _____.
- Define amplitude of an A.C.

SECTION-B

Note: Short answer type questions. Attempt any ten parts (10x4=40)

- Q.2
- Give advantage of electric energy over other forms of energy.
 - Explain kirchhoff's voltage law.

HSBTEonline.com

(2)

120828

- iii) Explain difference between A.C. and D.C. HSBTEonline.com
- iv) Define maximum power transfer theorem.
- v) Write reactions that take place during charging and discharging at anode and cathode in lead acid cell.
- vi) Give similarity between electric circuit and magnetic circuit.
- vii) Define Faraday's laws of electro magnetic induction.
- viii) Draw and explain Impedance triangle.
- ix) Explain series and parallel connection of resistances.
- x) Explain Delta to star conversion.
- xi) Explain nickel cadmium cell.
- xii) Explain when A.C is applied to pure inductor.
- xiii) Explain advantage of Hydro power plant.
- xiv) Explain effect of temperature on resistance of a wire or conductor.
- xv) Explain Kirchhoff's current law.

HSBTEonline.com

SECTION-C HSBTEonline.com

Note: Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 State & explain thevenin theorem with example.
- Q.4 An A.C. voltage is given by $v=200 \sin 314t$. find its amplitude, frequency, time period and value of v when $t=0.005$ sec.
- Q.5 Draw block diagram of thermal power plant.
- Q.6 An A.c voltage of 230V, 50 Hz is applied across a resistance of 100Ω and inductance of 0.1 Henry in series. Calculate impedance of circuit current power factor and power consumed.
- Q.7 Explain the concept of Ideal and practical voltage source and current source, their symbolic and graphical representation.

HSBTEonline.com