

SECTION-C

Note: Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 Explain principle of working of complementary symmetry push pull amplifier.
- Q.4 What are typical feedback circuits? Draw potential divider feedback circuit and collector base voltage feedback circuit.
- Q.5 Explain diagram and working of wein's bridge oscillator circuit.
- Q.6 Explain the working of transistor inverter circuit using power transistors.
- Q.7 Explain basic operational amplifier. Name different basic amplifier applications.

No. of Printed Pages : 4

Roll No.

127543

4th Sem. / Fire Technology and Safety

Subject : Electronic Devices and Circuits

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1 a) What is the use of voltage amplifier?
- b) Define power dissipation capability.
- c) Efficiency of class B amplifier is _____ than that of class A amplifier.
- d) Define harmonic distortion.
- e) Class C amplifiers are used as _____.
- f) In push-pull arrangement, when one transistor is ON, the other is OFF and vice versa. (True/ False)
- g) Define tuned amplifier.
- h) Define quality factor.

(80)

(4)

127543

(1)

127543

- i) What is frequency response?
- j) Voltage gain of an amplifier with negative feedback is given by _____.
- k) Define Oscillator.
- l) Define piezoelectric crystal.
- m) Draw rectangular waveform.
- n) Transistor can be employed as a switch. (True / False)
- o) What is diode?
- p) Full form of CVT is _____.
- q) Which IC is used as voltage regulator?
- r) IC555 has _____ number of pins.

SECTION-B

Note: Short answer type questions. Attempt any ten parts
10x4=40

- Q.2 i) What is the use of heat sink in the power amplifier?

(2)

127543

- ii) What are the advantages of push pull amplifier circuit?
- iii) What are the applications of tuned voltage amplifiers?
- iv) What is the importance of positive feedback in amplifiers?
- v) What are the limitations of LC oscillators?
- vi) What are the essentials of an oscillator?
- vii) Write a short note on "Crystal oscillator circuit".
- viii) Define and draw an integrating circuit.
- ix) What are different applications of wave shaping circuits?
- x) What is bi-stable multivibrator circuit?
- xi) What are different types of power supply?
- xii) Write a short note on "SMPS".
- xiii) Draw block diagram of IC 555.
- xiv) What is differential amplifier? Explain.
- xv) Draw pin configuration of IC 741.

(3)

127543