

- xiv) Explain the details of IC 7495.
- xv) What is the working principle of D/A converters?

SECTION-C

Note: Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 What is digital signal? What are various advantages of digital signal? Also write different applications of digital signals.
- Q.4 Explain four bit decoder circuit for 7-Segment display with the help of suitable diagram.
- Q.5 Explain the working of 3-bit up/down synchronous counter with the help of truth diagram.
- Q.6 Draw diagram and explain working principle of Stair step ramp A/D converter.
- Q.7 Find out the minimum expression for function using K-Map

$$Y(A,B,C,D) = \sum m(0,1,2,3,10,12) + \sum d(4,8)$$

(400) (4) 121536/031536

No. of Printed Pages : 4 121536/031536
 Roll No.

3rd Sem. / IC/ EI

Subject : Fundamentals of Digital Electronics

Time : 3 Hrs. M.M. : 100

SECTION-A

Note: Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1 a) What is difference between analog and digital signal?
- b) Define Byte.
- c) Convert octal number $(763)_8$ into equivalent binary number.
- d) What do you mean by 2's complement?
- e) _____ code is an example of non-weighted code.
- f) Convert BCD number 01010001 into decimal number.
- g) Binary number 101011100001 has even parity. (True/False)

(1) 121536/031536

- h) Define logic gate.
- i) VLSI consists of _____ number of gates.
- j) CMOS stands of _____.
- k) $X.(X+Y)=$ _____.
- l) Define K- map.
- m) What is difference between half adder and full adder circuit?
- n) Define DEMUX.
- o) Name any IC used for flip flops.
- p) Define asynchronous counter.
- q) Draw diagram of Parallel in serial out shift register.
- r) Name any two performance characteristics of D/A converters.

SECTION-B

Note: Short answer type questions. Attempt any ten parts 10x4=40

Q.2 i) Explain Octal and Hexadecimal numbers.

(2) 121536/031536

- ii) What will be the result after dividing $(11011)_2$ by $(101)_2$?
- iii) What is gray code? How to convert gray code to binary code?
- iv) Explain the concept of parity. What is single and double parity?
- v) What are universe gates? Name logic gates which are used as universe gate.
- vi) Draw symbol of AND gate. Also explain truth table of AND gate.
- vii) Write a short note on " CMOS logic family".
- viii) Explain De Morgan's theorems.
- ix) What are three basic laws of Boolean algebra?
- x) Draw and explain 4 bit full adder circuit.
- xi) Explain basic functions of MUX with the help of diagram.
- xii) Explain the operation of RS flip flop with the help of truth table.
- xiii) Write a short note on "Divide by N ripple counters".

(3) 121536/031536