

No. of Printed Pages : 4

Roll No.

120933/30933

3rd Sem. / Electrical / GE / PE

Subject : Basic Electronics -I/BE

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note:Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1
- a) Ideal Diode
 - b) Constant Voltage Source
 - c) Conductivity of silicon
 - d) Ripples
 - e) MOSFET
 - f) Varactor Diode
 - g) DC Load line
 - h) Decibel Gain
 - i) Limitation at direct coupled amplifier

(1)

120933/30933

- j) Transistor Biasing
- k) H-Parameters
- l) Atomic Structure
- m) Drift Current
- n) Passive Components
- o) Junction Breakdown
- p) Input impedance
- q) Junction Transistor
- r) Potential barrier.

SECTION-B

Note:Short answer type questions. Attempt any ten parts 10x4=40

- Q.2
- i) Discuss atomic structure of silicon.
 - ii) Explain series inductor filter
 - iii) Explain CE configuration of transistor .
 - iv) Explain types of active components.

(2)

120933/30933

- v) Explain concept of AC Load line.
- vi) Why silicon is preferred to other semiconductor.
- vii) Short note on photo diode & its applications
- viii) Explain half wave rectifier using diodes.
- ix) Define operating point & why there is need of stabilization of operating point.
- x) Explain transformer coupled amplifiers.
- xi) Operating and characteristics of N Channel JEET.
- xii) What are Electronic components & its types.
- xiii) Explain the process of generation and recombination of electron hole pairs.
- xiv) What is the concept of junction capacitance in forward and reverse biased conditions.
- xv) Explain intrinsic semiconductors & its types.

(3) 120933/30933

SECTION-C

Note: Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 Draw the A.C. equivalent circuit of single stage transistor amplifiers and frequency response in amplifiers. Explain
- Q.4 Explain V-I characteristics of semiconductor diode and static resistance
- Q.5 Differentiate between Intrinsic and Extrinsic semiconductor
- Q.6 What is transistor biasing. Name the different methods used in biasing and their advantages.
- Q.7 Write short note on :
 - i) Loading effect in multistage amplifiers
 - ii) Compare BJT, JEET & MOSFET.

(6620) (4) 120933/30933