

No. of Printed Pages : 4

Roll No. 120953/030953/105853

5th Sem. / Elect. / P.S. Engg. / Elect & Eltx. Engg.

Subject : Industrial Electronics and Control of Drives

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1
- a) What are number of PN junction in a Thyristor?
 - b) What is Heat Sink?
 - c) What is LASCR?
 - d) Draw the symbol for TRIAC.
 - e) Define Controlled rectifier.
 - f) In a three phase full wave half controlled converter, the thyristors are fired at an interval of _____.
 - g) What is full form of UJT.
 - h) Current source inverter is _____ of load.

(1) 120953/030953/105853

- i) What is a chopper?
- j) What is class A chopper?
- k) Define Cycloconverter.
- l) Define Heat sink.
- m) In a load acid cell, active material for +ve plate is _____.
- n) What is an Online UPS?
- o) What is Commutation.
- p) Draw the symbol of SCR.
- q) Voltage source inverter, allows a variable frequency supply to be obtained from a _____ source. (AC / DC).
- r) Draw V-I characteristics of TRIAC.

SECTION-B

Note: Short answer type questions. Attempt any ten parts 10x4=40

- Q.2
- i) What is thyristor string? Define string efficiency.

(2) 120953/030953/105853

- ii) What are different methods of triggering?
- iii) Explain the speed control of fax regulator using thyristor with the help of diagram.
- iv) What is forced commutation & natural commutation?
- v) Differentiate between ON-LINE UPS and OFF-LINE UPS.
- vi) What are the indications of fully charged cell.
- vii) Draw block diagram of electric drive. Explain.
- viii) Write a short note on static control of drive.
- ix) Explain the thyristor control of half wave dc drive.
- x) What is the difference between voltage source and current source inverter?
- xi) How choppers are classified on the basis of their operation in any of four quadrants?
- xii) Draw the block diagram of an inverter and explain its working.

(3) 120953/030953/105853

- xiii) Draw the circuit diagram for three phase dual converter.
- xiv) State few applications in which controlled DC is required.
- xv) Draw the circuit diagram of three phase half controlled bridge rectifier.

SECTION-C

Note: Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 Draw and explain V-I characteristics of SCR.
- Q.4 Draw the circuit diagram and explain working of single phase half wave controlled rectifier with resistive load.
- Q.5 Draw the circuit diagram of single phase cycle converter and explain its working.
- Q.6 Describe briefly the slip control of AC drives.
- Q.7 What are important instructions necessary for the maintenance & care of Lead Acid cells?

(3380)

(4) 120953/030953/105853